



## Wilkinson Power Divider $Z_0=50$ ohm $F_0=10$ MHz

Note: This is a low-Q circuit, so you can use nearest preferred values.  
For example; 1  $\mu$ H / 220 pF / 470 pF

More info: [http://rfdesignn.com/mag/radio\\_designing\\_lc\\_wilkinson/](http://rfdesignn.com/mag/radio_designing_lc_wilkinson/)